

Khulna University of Engineering & Technology

Report on Smart Home Project

Course No : CSE 3104

Course Name: Peripherals and Interfacing Laboratory

Project Name: Smart Home Project

Project Partners: 1707038, 1707040, 1707060

Submitted To

Dr. Md. Sheikh Sadi Sir

Professor

Dept. of Computer Science and Engineering

KUET – 9203

S.M Taslim Uddin Raju Sir

Lecturer

Dept. of Computer Science and Engineering

KUET – 9203

Submitted By

Md. Jibon Mia (1707038),

Rahat Mahmud Khan (1707040),

Md. Rakib Hossain (1707060),

Dept. of Computer Science and Engineering

Batch 2k-17

KUET - 9203

Objective:

The main objective of this project is to make home users life easier. Using the circuit of this project, home users don't need to go to their main circuit board to ON/OFF their AC appliances like LEDs, TVs, FANs etc. Users can control their ac appliances using Bluetooth software along with this project circuit in any suitable place inside their home.

Introduction:

This is a smart home project that will help a home user to control home appliances like LEDs, TV, FANs i.e any AC appliances wirelessly means using software that uses Bluetooth connection to the project circuit.

Components:

1. 4 channels Relay Module
2. Arduino Uno
3. HC05 Bluetooth Module
4. Bluetooth Software like 'Arduino Bluetooth Controller (4 channel)'
5. AC components like Bulbs
6. Jumper wires
7. Breadboard and Arduino Program.

Connection Steps:

1. There are 6 pins in the Relay Module: Gnd, Vcc, IN-1, IN-2, IN-3, IN-4
 - a. IN-1 for Relay1
 - b. IN-2 for Relay2
 - c. IN-3 for Relay3
 - d. IN-4 for Relay4
2. Connect input pins IN-1/2/3/4 to arduino's pin 2/3/4/5
3. Connect Bluetooth module's TX and RX pins to arduino's pin 10, 12
4. Connect arduino's Gnd and 5v pins to breadboard's Gnd and Vcc
5. Connect Gnd, Vcc of both Relay module and Bluetooth module to breadboard's Gnd and Vcc pin.
6. Each relay has 3 pins: NC, COMMON, NO
7. Connect relays to AC power supply and AC components like the following
 - a. Power supply's Positive Terminal + each relay's COMMON pin (by sorting)
 - b. Each AC component's Positive Terminal + each relay's NO (Normal Open) pin
 - c. Sort all the negative terminals of both Power Supply and AC Components together

Working Principle:

1. We used an app called "Bluetooth Controller 4CH"
2. First we have to make connection between this APP and Bluetooth Module (HC-05)
3. 6 buttons are there (button 1, 2, 3, 4, ON ALL and OFF ALL) in the app
4. When button-1 is pressed 1st time, character value '1' is passed to Bluetooth module that receives the value by RX pin, which then send to Arduino through TX pin
5. So according to the program inside Arduino, the AC component connected to Relay-1 will be ON
6. When button 1 is pressed again, character value 'A' is passed and the AC component connected to Relay-1 will be OFF
7. Similarly for buttons 2,3,4 character values '2', '3', '4' are passed for 1st press and 'B', 'C', 'D' are passed for 2nd press.
8. For button-ON ALL, character value '9' passed and all AC components connected to 4 relays will be ON
9. For button-OFF ALL, character value 'I' passed and all AC components connected to 4 relays will be OFF

Arduino Program (4 channel):

/**

* Relay IN1 = pin-2 of Arduino

* Relay IN2 = pin-3 of Arduino

* Relay IN3 = pin-4 of Arduino

* Relay IN4 = pin-5 of Arduino

*/

#include<SoftwareSerial.h>

SoftwareSerial mySerial(10, 12); // Arduino's 10 = TX and 12 = RX pin of Bluetooth Module(HC-05) Model.

```
#define relay1 2
```

```
#define relay2 3
```

```
#define relay3 4
```

```
#define relay4 5
```

```
char val;
```

```
void setup() {
```

```
    // put your setup code here, to run once:
```

```
    pinMode(relay1,OUTPUT);
```

```
    pinMode(relay2,OUTPUT);
```

```
    pinMode(relay3,OUTPUT);
```

```
    pinMode(relay4,OUTPUT);
```

```
    //Initially, all relays are off, HIGH = OFF, LOW = ON
```

```
    digitalWrite(relay1,HIGH);
```

```
    digitalWrite(relay2,HIGH);
```

```
    digitalWrite(relay3,HIGH);
```

```
    digitalWrite(relay4,HIGH);
```

```
    mySerial.begin(9600);
```

```
    Serial.begin(9600);
```

```
}
```

```
void loop() {
```

```
    //check data serial from bluetooth android App
```

```
    if( mySerial.available() > 0 ) {
```

```
        val = mySerial.read();
```

```
        Serial.println(val);
```

```
    }
```

```
    //Relay1 is on
```

```
    if( val == '1' ) {
```

```
        digitalWrite(relay1,LOW);
```

```
    }
```

```
    //Relay2 is on
```

```
    else if( val == '2' ) {
```

```
        digitalWrite(relay2,LOW);
```

```
    }
```

```
    //Relay3 is on
```

```
    else if( val == '3' ) {
```

```
        digitalWrite(relay3,LOW);
```

```
    }
```

```
//Relay4 is on  
  
else if( val == '4' ) {  
    digitalWrite(relay4,LOW);  
}
```

```
//All relays ON for '9'  
  
else if( val == '9' ) {  
    digitalWrite(relay1,LOW);  
    digitalWrite(relay2,LOW);  
    digitalWrite(relay3,LOW);  
    digitalWrite(relay4,LOW);  
}
```

```
//relay1 is off  
  
else if( val == 'A' ) {  
    digitalWrite(relay1,HIGH);  
}
```

```
//relay2 is off  
  
else if( val == 'B' ) {  
    digitalWrite(relay2,HIGH);  
}
```

```
//relay3 is off

else if( val == 'C' ) {

    digitalWrite(relay3,HIGH);

}


//relay4 is off

else if( val == 'D' ) {

    digitalWrite(relay4,HIGH);

}


//all relays off for 'I'

else if( val == 'I' ) {

    digitalWrite(relay1,HIGH);

    digitalWrite(relay2,HIGH);

    digitalWrite(relay3,HIGH);

    digitalWrite(relay4,HIGH);

}

}
```

Discussion:

So that's how we implemented our project that will definitely make people lives easier, most importantly it will save their time in a great amount. It's easy to understand the circuit board, connection and programming to control the AC components but at the end it's a great

satisfaction when we ON/OFF the AC components using software and Bluetooth connection. Although Bluetooth module, relay module are a little bit expensive but we managed them.

Conclusion:

We did the project in a simple way. But for larger system/events, this project can be done in smarter way than we did here. We can use relay modules with a great number of relays and Bluetooth circuit that may contain many Bluetooth modules. So it depends on the requirements, budget and the environment. However projects like this one will definitely make people lives much more easier than ever before.